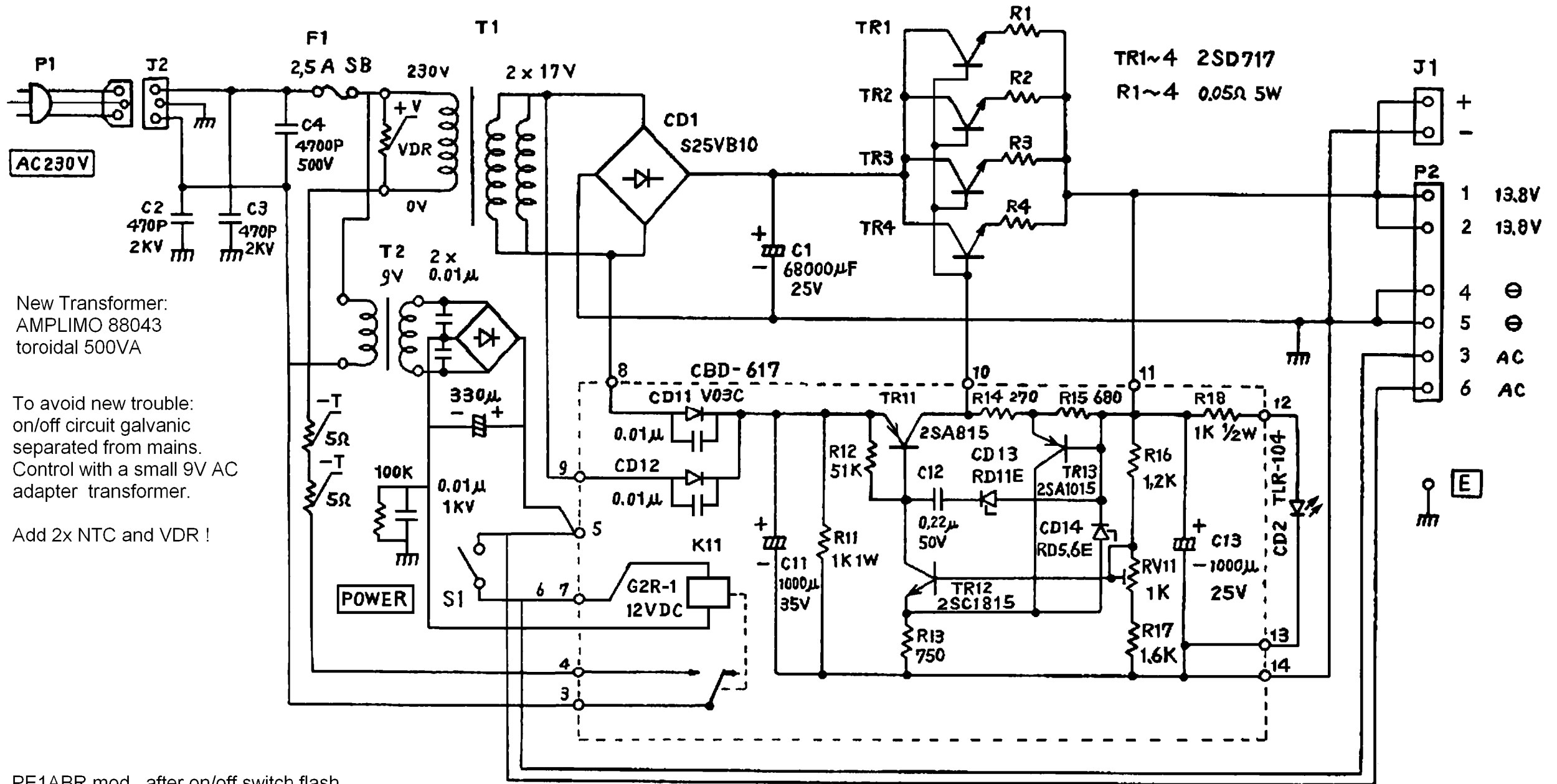




New Transformer:
AMPLIMO 88043
toroidal 500VA

To avoid new trouble:
on/off circuit galvanic
separated from mains.
Control with a small 9V AC
adaptor transformer.

Add 2x NTC and VDR !

PE1ABR mod, after on/off switch flash
over to ground and transformer breakdown
and burnt out due to overvoltage

If heat becomes too high, add 2 to 3 anti voltage windings
(= 1 to 1,5 V lower output AC)

JRC NBD-500 Power Supply